

VLSI Project Report

Soham Jahagirdar


2023102046

IIIT Hyderabad

soham.jahagirdar@students.iiit.ac.in

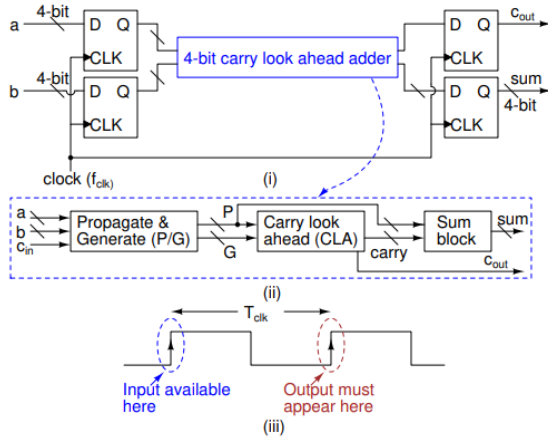I. INTRODUCTION

A 4-bit Carry Look-Ahead (CLA) Adder computes the sum of two 4-bit numbers and outputs a 4-bit sum with a 5th carry bit. Unlike a Ripple Carry Adder, which calculates carries sequentially, the CLA Adder determines all carries simultaneously, minimizing propagation delay.



CLA Block Diagram

II. PROPOSED STRUCTURE FOR CLA

We need to create Three Blocks that are Carry(c_i), Propagate(p_i) and Generate(g_i)

p_i and g_i are given by

$$p_i = a_i \oplus b_i$$
$$g_i = a_i * b_i$$

Then we use Propagate and Generate to calculate Carry
 $c_{i+1} = p_i * c_i + g_i$


Finally we get all the carries as-

$$c_1 = (p_0 * c_0) + g_0$$
$$c_2 = (p_1 * p_0 * c_0) + (p_1 * g_0) + g_1$$
$$c_3 = (p_2 * p_1 * p_0 * c_0) + (p_2 * p_1 * g_0) + (p_2 * g_1) + g_2$$
$$c_4 = (p_3 * p_2 * p_1 * p_0 * c) + (p_3 * p_2 * p_1 * g_0) + (p_3 * p_2 * g_1) + (p_3 * g_2) + g_3$$

And the final Sum can be calculated as

$$S_i = p_i \oplus c_i$$

 Now we represent the above circuit as Combination of 2-i/p AND,OR and XOR Gates




CLA Circuit Diagram


III. TOPOLOGY AND SIZING

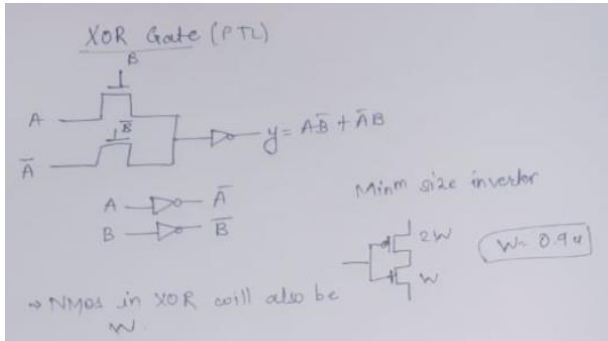A. CLA Combinational Circuit


We need 2-input AND, OR and XOR gates for designing the proposed Circuit. AND, OR gates and Inverters are made using CMOS Style and XOR is made using PTL Logic style.



XOR Gate

 


AND Gate

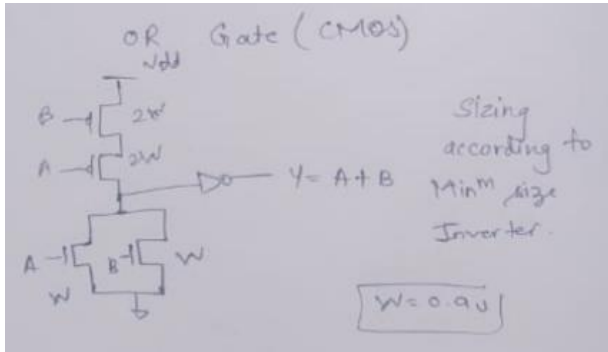

OR Gate

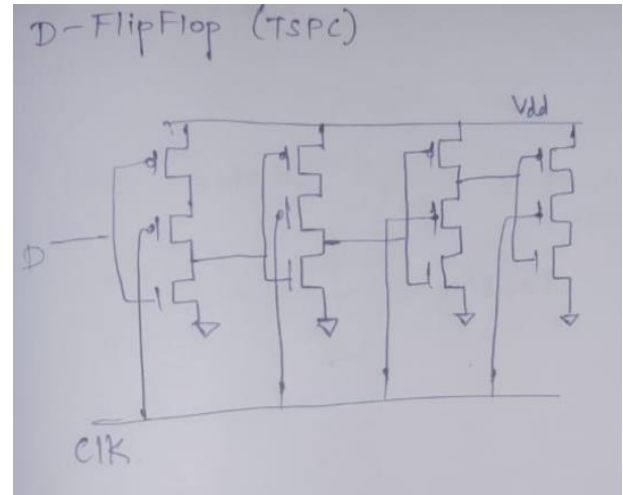B. D-FlipFlop

We use a TSPC D-flipflop working on Positive Edge. PMOS Width = 40W and NMOS Width = 20W




TSPC D-FlipFlop

IV. PRE-LAYOUT SIMULATIONS IN NGSPICE

 A. CLA Combinational Circuit

For eg, we take inputs as 1001 and 0110 and we get output as 0111, hence we verify the working of CLA Circuit in NgSpice.




Now to calculate Propagation Delay we give all Inputs as 1 .i.e a=1111,b=1111 , including Cin. So, we get the Delays as Below

tpd_carry	=	1.670580e-10	targ=	2.170580e-10	trig=	5.000000e-11
tpd_s3	=	2.674000e-10	targ=	3.174000e-10	trig=	5.000000e-11
tpd_s2	=	2.668316e-10	targ=	3.168316e-10	trig=	5.000000e-11
tpd_s1	=	3.089448e-10	targ=	3.589448e-10	trig=	5.000000e-11
tpd_s0	=	5.456553e-11	targ=	1.045655e-10	trig=	5.000000e-11

We have $T_{pd(max)}=0.3089$ ns and $T_{pd(min)}=54.55$ ps.

B. D-FlipFlop

 

Finding T_{PCQ} of the FlipFlop

```
tpcq_min      = 1.153144e-10 targ= 2.316531e-08 trig= 2.305000e-08
tpcq_max      = 1.579699e-10 targ= 3.207970e-09 trig= 3.050000e-09
```

V. TIMING ANALYSIS

A.D-Flipflop


As we have used a TSPC topology while Designing the Flipflop as there is no $\sim clk$ involved T_{HOLD} of our Flipflop is zero.

By Hit and Trial we observe that if clock comes before 0.111ns we don't get an output, hence $T_{SETUP}=0.111$ ns.

B.Finding Maximum Clock Frequency

$$\begin{aligned} T_{CLK(min)} &= T_{SETUP} + T_{PD(max)} + T_{PCQ(max)} \\ &= 0.111 + 0.3089 + 0.1579 \text{ ns} \\ &= 0.5778 \text{ ns} \end{aligned}$$

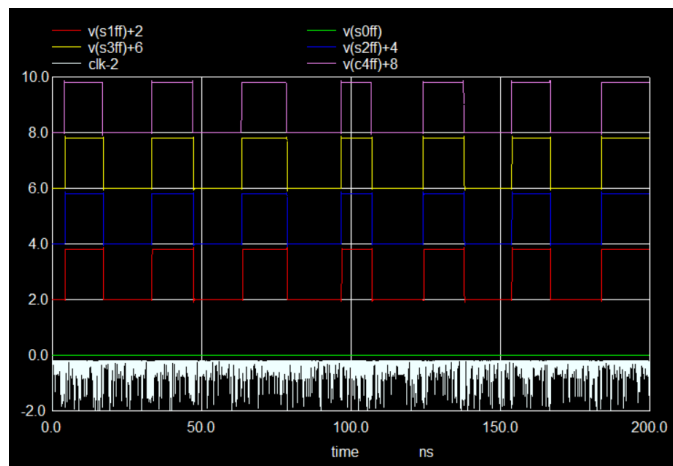
$$F_{CLK(max)} = 1 / T_{CLK(min)} = 1.73 \text{ GHz}$$




Output at $T_{CLK}=0.6$ ns

We get Reliable Results at $T_{CLK}=0.6$ ns which is quite close to our theoretical Calculations.


VI. STICK DIAGRAMS FOR UNIQUE COMPONENTS

 


XOR GATE

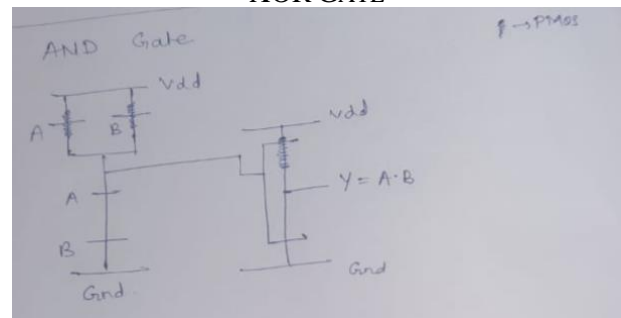

AND Gate

 

OR Gate


 


D FlipFlop

VII. POST LAYOUT SIMULATIONS

A. CLA Combinational Circuit

Magic Layout-

 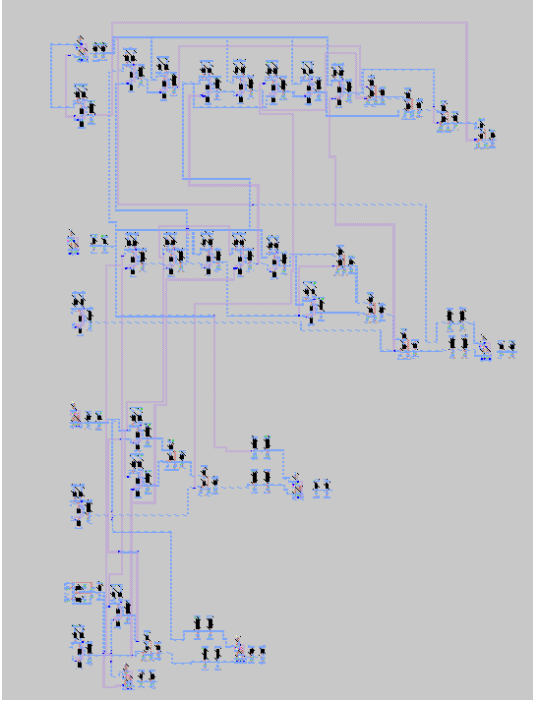

CLA output for a=1111/0111 and b=1111/0111


Now to calculate Propagation Delay we give all Inputs as 1 i.e a=1111,b=1111 , including Cin. So,we get the Delays as Below

No. of Data Rows : 10016

Measurements for Transient Analysis

tpd_carry	=	1.548711e-10	targ=	1.598711e-10	trig=	5.000000e-12
tpd_s3	=	4.306739e-10	targ=	4.356739e-10	trig=	5.000000e-12
tpd_s2	=	3.868852e-10	targ=	3.918852e-10	trig=	5.000000e-12
tpd_s1	=	4.080594e-10	targ=	4.130594e-10	trig=	5.000000e-12
tpd_s0	=	1.077756e-10	targ=	1.127756e-10	trig=	5.000000e-12

 First,we test the same input that we used Pre-Layout i.e 1001 and 0110



CLA output for a=1001 and b=0110


Our CLA is working fine Post-Layout.


Lets Take more case as 0111,0111 and 1111,1111 we can verify the output is 01110 and 11110.Hence, our CLA is functioning Properly.

We have $T_{pd(max)}=0.430$ ns and $T_{pd(min)}=0.154$ ns

B. D-FlipFlop

Magic Layout-

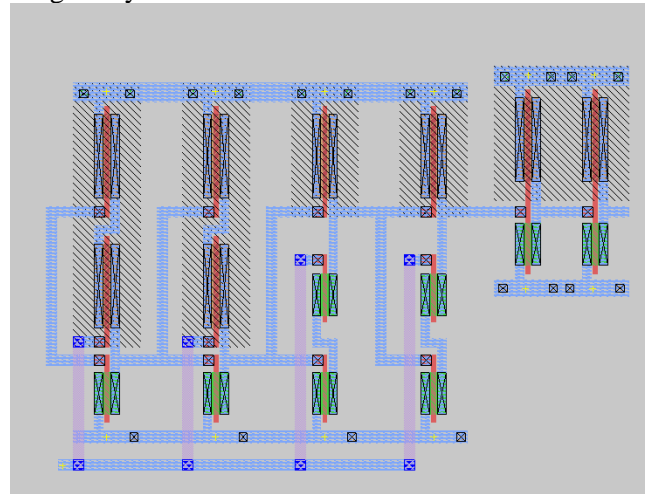

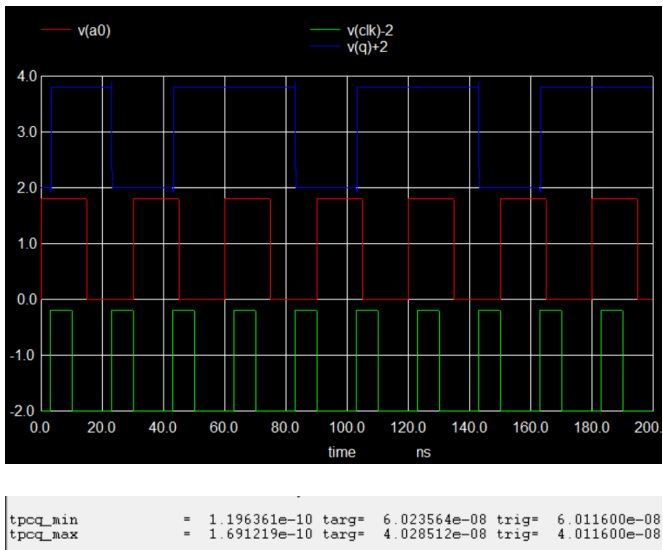


As we have used a TSPC topology while Designing the Flipflop as there is no $\sim\text{clk}$ involved T_{HOLD} of our Flipflop is zero.

By Hit and Trial we observe that if clock comes before 0.111ns we don't get an output, hence $T_{\text{SETUP}}=0.117\text{ns}$.

Finding Maximum Clock Frequency

$$\begin{aligned}
 T_{\text{CLK}}(\text{min}) &= T_{\text{SETUP}} + T_{\text{PD}}(\text{max}) + T_{\text{PCQ}}(\text{max}) \\
 &= 0.117 + 0.430 + 0.1691 \text{ ns} \\
 &= 0.7161 \text{ ns}
 \end{aligned}$$
 
$$F_{\text{CLK}}(\text{max}) = 1 / T_{\text{CLK}}(\text{min}) = 1.39 \text{ GHz}$$




Output at $T_{\text{CLK}}=0.9\text{ns}$


We find for the inputs $a=1111$ and $b=1111$ we find Reliable Outputs for $T_{\text{CLK}}=0.9 \text{ ns}$.

C. Final Circuit

Magic Layout-

 

 Let's Take test case as 0111,0111 and 1111,1111 we can verify the output is 01110 and 11110. Hence, our CLA is functioning Properly



Output for $a=0111/1111$ and $b=0111/1111$

+256.32 +283.68 microns

Horizontal Pitch=256.32 μm

Vertical Pitch=283.68 μm

VIII. PRE AND POST LAYOUT COMPARISONS

	Pre Layout	Post Layout
$T_{PD(max)}$	0.3089 ns	0.430 ns
$T_{PD(min)}$	0.054 ns	0.154 ns

	Pre Layout	Post Layout
$T_{PCQ(max)}$	0.157 ns	0.169 ns
$T_{PCQ(min)}$	0.115 ns	0.119 ns

	Pre Layout	Post Layout
$F_{CLK(max)}$ theoretical	1.73 GHz	1.39 GHz
$F_{CLK(max)}$ observed	1.66 GHz	1.11 GHz


IX. VERILOG SIMULATIONS

We test the Verilog Circuit with inputs
a=1111,b=1111 and a=0110,b=1001

Reset = 0	A = 1111	B = 1111	Cout = 0	S = 0000
Reset = 0	A = 1111	B = 1111	Cout = 1	S = 1110
Reset = 0	A = 0110	B = 1001	Cout = 1	S = 1110
Reset = 0	A = 0110	B = 1001	Cout = 0	S = 1111

Verilog Output

 Now plotting the Waveform of these Outputs



GTKWave Output

We can Observe that after input comes, we get output on next +ve clock edge. $15+15=11110$ and $6+9=01111$

X. FPGA SIMULATION


We give input as 7 and 10 in FPGA



FPGA Output

We can see the output 10001(17).

 Now we also Verify the Reading using Oscilloscope.




Oscilloscope Outputs

Oscilloscope Readings:


Output > 3.2V is considered high i.e 1



Cout=1

 

S3=0 and S2=0

 

S1=0 and S0=1

The output is 10001.

ACKNOWLEDGMENT

I would like to express my gratitude to **Prof. Abhishek Srivastava** and VLSI-D TAs for their invaluable guidance and mentorship throughout the course and this project.

REFERENCES

- [1] Digital Logic and Computer Design by Morris Mano
- [2] Verilog HDL - Samir Palnitkar
- [3] Various IEEE Papers